

Digital Systems Design and Laboratory

[7. Multi-Level Gate Circuits]

Chung-Wei Lin

cwlin@csie.ntu.edu.tw

CSIE Department

National Taiwan University

Spring 2019

Recap: Logic Design

□ Steps

- Translate the word description into a switching function (Unit 4)
 - Truth table
 - Boolean expression
 - SOP/POS derived from minterm or maxterm expansion (Unit 4)
- Simplify the function
 - Boolean algebra (Units 2 and 3)
 - Karnaugh map (Unit 5)
 - Quine-McCluskey (Unit 6)
 - Other methods
- Realize it using available logic gates
 - AND-OR, OR-AND (Unit 2)
 - NAND-NAND, NOR-NOR (Unit 7)
 - Others

Outline

☐ **Multi-Level Gate Circuits**

- ☐ NAND and NOR Gates
- ☐ Two-Level NAND- and NOR-Gate Circuits
- ☐ Multi-Level NAND- and NOR-Gate Circuits
- ☐ Circuit Conversion Using Alternative Gate Symbols
- ☐ Design of Two-Level, Multiple-Output Circuits
- ☐ Multiple-Output NAND and NOR Circuits


AND-OR & OR-AND Circuits

❑ The # of levels in a circuit = the maximum # of gates cascaded in series between an input & the output

- Count from the output
- Do NOT count inverters at inputs

❑ Two-level circuits learned so far

 
- AND-OR circuit = SOP form
 - One level of AND gates + one OR gate
- OR-AND circuit = POS form
 - One level of OR gates + one AND gate



OR-AND-OR & AND-OR-AND Circuits

□ Three-level circuits


- OR-AND-OR circuit
- AND-OR-AND circuit

 

One More Example (1/2)

□ How to count the # of levels?

 - By inspection
- Example: $Z = (AB + C)(D + E + FG) + H$
 - 4 levels
 - 6 gates
 - 13 gate inputs




One More Example (2/2)

□ Same function in another realization

➤ $Z = AB(D + E) + C(D + E) + ABFG + CFG + H$

- 3 levels
- 6 gates
- 19 gate inputs

 


Multi-Level Gate Circuits

❑ Q1: Why does the # of levels matter?

❑ A1: The # of levels affects cost and delay

 - Cost depends on # of gates & # of gate inputs
- Delay depends on # of levels & # of inputs for a single gate
- # of levels \uparrow : cost \downarrow (maybe) and circuit delay \uparrow (maybe)



❑ Q2: Any application for the level of each gate?

❑ A2: Evaluation according to the level in nonincreasing order

❑ Q3: How to change the # of levels?

❑ A3: Factoring or multiplying out

Multi-Level Design with AND & OR (1/4)

□ Find a circuit of AND and OR gates to realize

➤ $F(A,B,C,D) = \sum m(1, 5, 6, 10, 13, 14)$


□ Solution 1: try two-level AND-OR circuit first

➤ Simplify f by K-map (circle 1's)

➤ Realize it

CD \ AB	00	01	11	10
00				
01	1	1	1	
11				
10		1	1	1

$$F = A'C'D + BC'D + BCD' + ACD'$$

 

Multi-Level Design with AND & OR (2/4)

❑ From Solution 1


➤ $F = A'C'D + BC'D + BCD' + ACD'$

❑ Solution 2

➤ Factoring it yields $F = (A' + B)C'D + (B + A)CD'$

➤ Lead to a three-level OR-AND-OR circuit

 - # of gate inputs ↓, cost ↓ (maybe), delay ↑ (maybe)



3 Levels
5 Gates
12 Gate Inputs

Multi-Level Design with AND & OR (3/4)

□ Find a circuit of AND and OR gates to realize

➤ $F(A,B,C,D) = \sum m(1, 5, 6, 10, 13, 14)$


□ Solution 3: try two-level OR-AND circuit first

➤ Simplify f by K-map (circle 0's)

➤ Realize it

AB \ CD	00	01	11	10
00	0	0	0	0
01	1	1	1	0
11	0	0	0	0
10	0	1	1	1
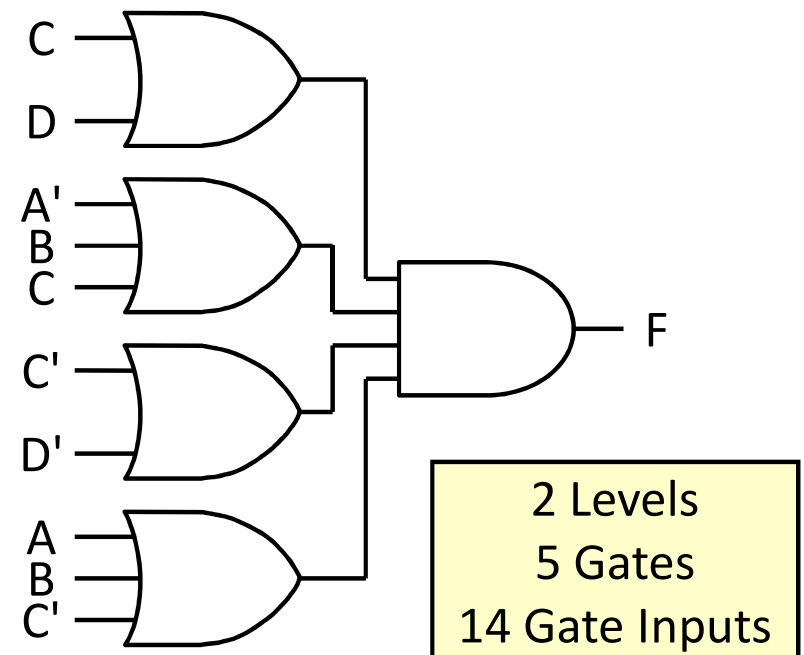
$$F' = C'D' + AB'C' + CD + A'B'C$$
$$F = (C + D)(A' + B + C)(C' + D')(A + B + C')$$



Multi-Level Design with AND & OR (4/4)

❑ From Solution 3


➤ $F = (C + D)(A' + B + C)(C' + D')(A + B + C')$

❑ Solution 4

- Multiplying it out yields $F = [C + D(A' + B)][C' + D'(A + B)]$ (4-level)
- Partially multiplying out yields $F = (C + A'D + BD)(C' + AD' + BD')$
- Lead to a three-level AND-OR-AND circuit

❑ Best solutions for F

 - Two-level: OR-AND
- (Solution 3)
- Three-level: OR-AND-OR
- (Solution 2)




Outline

- ❑ Multi-Level Gate Circuits
- ❑ **NAND and NOR Gates**
- ❑ Two-Level NAND- and NOR-Gate Circuits
- ❑ Multi-Level NAND- and NOR-Gate Circuits
- ❑ Circuit Conversion Using Alternative Gate Symbols
- ❑ Design of Two-Level, Multiple-Output Circuits
- ❑ Multiple-Output NAND and NOR Circuits

NAND Gate

□ $\text{NAND} \equiv \text{AND-NOT}$

 
- DeMorgan's law: $F = (ABC)' = A' + B' + C'$
- General: $F = (X_1 X_2 \dots X_n)' = X_1' + X_2' + \dots + X_n'$
- Symbol: Bubble \equiv NOT



NOR Gate

□ NOR \equiv OR-NOT

 - DeMorgan's law: $F = (A + B + C)' = A'B'C'$
- General: $F = (X_1 + X_2 + \dots + X_n)' = X_1'X_2'\dots X_n'$
- Symbol: Bubble \equiv NOT



NAND & NOR Gates


- ❑ Actually, NAND & NOR are implemented by fewer switch devices and operate faster than AND & OR gates
 - Lower cost
 - Smaller delay

Functionally Complete Set (1/2)

□ A set of logic operations is functionally complete if any Boolean function can be expressed by this set

□ Examples



 
- Q1: {AND, OR, NOT}
- A1: Of course, yes!
- Q2: {AND, NOT}
- A2: Yes (check figure)
 - $X + Y = (X + Y)'' = (X'Y')'$
- Q3: {OR, NOT}
- A3: Yes (check figure)
 - $XY = (XY)'' = (X' + Y')'$
- Q4: {AND}
- Q5: {OR}



Functionally Complete Set (2/2)

□ Examples

   - Q6: {NAND}
- A6: Yes (check figure)
- Q7: {NOR}
- A7: Yes
- Q8: {AND, OR}



Outline

- ❑ Multi-Level Gate Circuits
- ❑ NAND and NOR Gates
- ❑ **Two-Level NAND- and NOR-Gate Circuits**
- ❑ Multi-Level NAND- and NOR-Gate Circuits
- ❑ Circuit Conversion Using Alternative Gate Symbols
- ❑ Design of Two-Level, Multiple-Output Circuits
- ❑ Multiple-Output NAND and NOR Circuits

Recap: DeMorgan's Law

□ General


- $(X_1 + X_2 + \dots + X_n)' = X_1'X_2'\dots X_n'$
- $(X_1X_2\dots X_n)' = X_1' + X_2' + \dots + X_n'$

□ One-step rule

- $[f(X_1, X_2, \dots, X_n, 0, 1, +, \bullet)]' = f(X_1', X_2', \dots, X_n', 1, 0, \bullet, +)$
 - $X \leftrightarrow X'$; $+ \leftrightarrow \bullet$; $0 \leftrightarrow 1$

□ Idea

 - Move "bubbles" and exchange AND gates and or gates




8 Basic Forms for 2-Level Circuits (1/2)

□ AND-OR \leftrightarrow AND-(NOT-NAND) \leftrightarrow NAND-NAND

□ NAND-NAND \leftrightarrow (NOT-OR)-NAND \leftrightarrow OR-NAND

□ OR-NAND \leftrightarrow OR-(NOT-OR) \leftrightarrow NOR-OR

 □ NOR-OR \leftrightarrow (NOT-AND)-OR \leftrightarrow AND-OR



8 Basic Forms for 2-Level Circuits (2/2)

□ OR-AND \leftrightarrow

OR-(NOT-NOR) \leftrightarrow

NOR-NOR \leftrightarrow

(NOT-AND)-NOR \leftrightarrow





AND-NOR \leftrightarrow

AND-(NOT-AND) \leftrightarrow

NAND-AND \leftrightarrow

(NOT-OR)-AND \leftrightarrow

OR-AND

    

Other Forms

❑ Other 8 forms are degenerated, i.e., cannot realize all switching functions

- AND-AND, AND-NAND
- OR-OR, OR-NOR
- NAND-OR, NAND-NOR
- NOR-AND, NOR-NAND

❑ Example

- $\text{NAND-NOR} \equiv \text{AND-AND} \dots$

Example: NAND-NAND & NOR-NOR

□ Procedure for designing a min 2-level NAND-NAND circuit

- Find a minimum SOP
- Draw AND-OR (2-level) circuit
- Convert into NAND-NAND circuit
 - Introduce 2 bubbles into each intermediate line or the output

□ Procedure for designing a min 2-level NOR-NOR circuit

- Find a minimum POS
- Draw OR-AND (2-level) circuit
- Convert into NOR-NOR circuit
 - Introduce 2 bubbles into each intermediate line or the output

□ Examples

- $F = A + BC' + B'CD$
- $F = (A + B + C)(A + B' + C')D$

Summary: 2-Level Logic Minimization

- ❑ Start with minimum SOP (AND-OR) or minimum POS (OR-AND)
 - Simplified: cost = (# of terms, # of literals) (Units 2--5)
 - Real: cost = (# of gates, # of gate inputs)
 - # of gates \leq # of terms + 1
 - # of gate inputs \leq # of literals + # of terms
 - "<" holds if a term is degenerated to a single variable
- ❑ Convert the min SOP (POS) to the target form
 - 8 basic forms can convert each other
 - DeMorgan's law
 - Use bubbles
- ❑ NAND/NOR gates: low cost & high speed

Stop Here (20190318)

Outline


- ❑ Multi-Level Gate Circuits
- ❑ NAND and NOR Gates
- ❑ Two-Level NAND- and NOR-Gate Circuits
- ❑ **Multi-Level NAND- and NOR-Gate Circuits**
- ❑ Circuit Conversion Using Alternative Gate Symbols
- ❑ Design of Two-Level, Multiple-Output Circuits
- ❑ Multiple-Output NAND and NOR Circuits

Multi-Level NAND-Gate Circuits

□ Procedure for designing a multi-level NAND circuit:

- Simplify the switching function
- Draw its multi-level AND-OR circuit
- Replace all gates with NANDs and number all levels (from the output)
- Invert inputs to levels 1, 3, 5, ...

 □ Example: $Z = A'[B' + C(D + E') + F'G'] + HI'J + K$








Outline


- ❑ Multi-Level Gate Circuits
- ❑ NAND and NOR Gates
- ❑ Two-Level NAND- and NOR-Gate Circuits
- ❑ Multi-Level NAND- and NOR-Gate Circuits
- ❑ **Circuit Conversion Using Alternative Gate Symbols**
- ❑ Design of Two-Level, Multiple-Output Circuits
- ❑ Multiple-Output NAND and NOR Circuits

Alternative Gate Symbols

     
- ❑ Do **NOT** memorize these gate symbols
- ❑ DeMorgan's law is the key of conversion
 - Use bubbles adequately



Example from OR-AND to NOR Gates

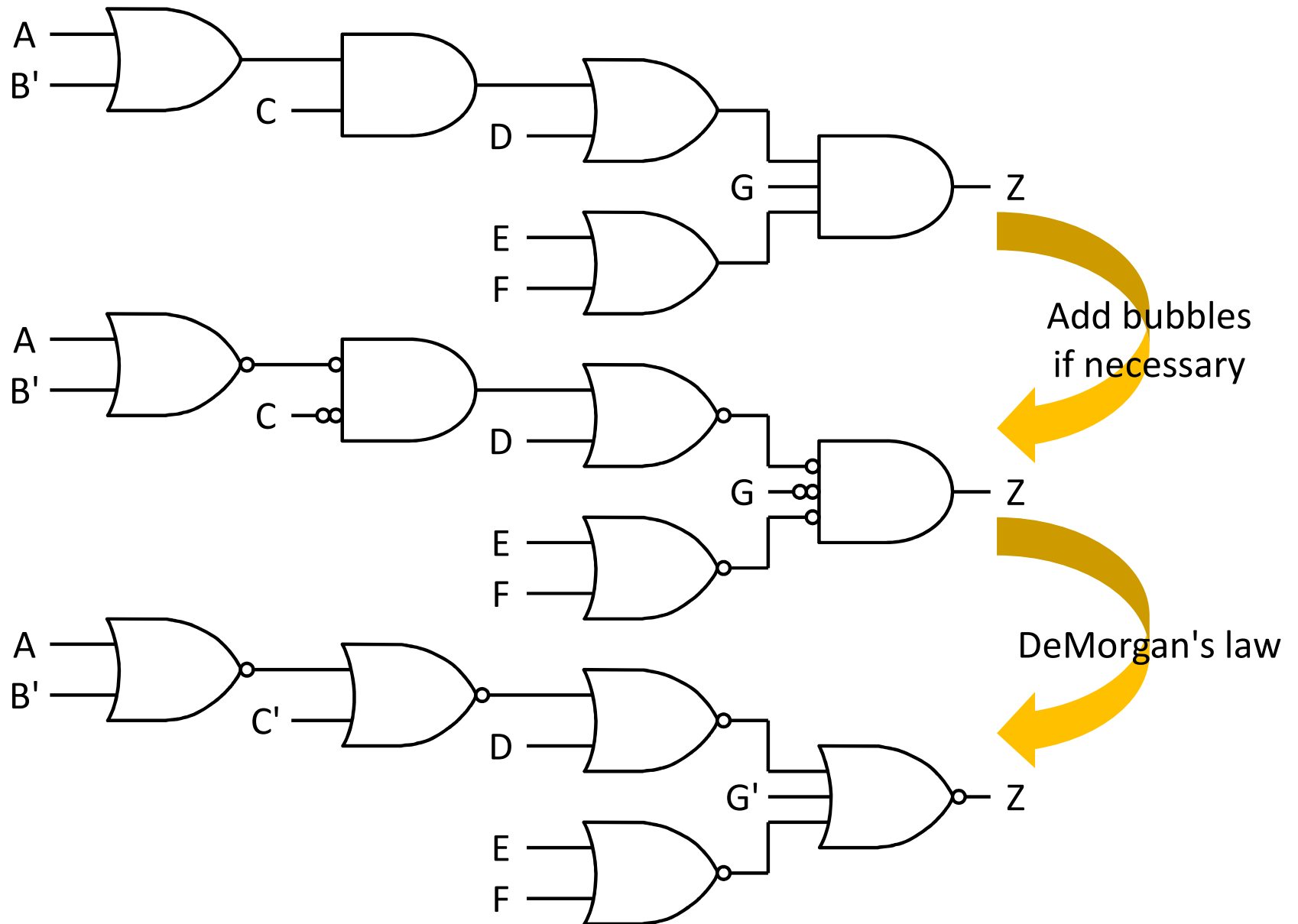

Example from NAND to AND-OR Gates

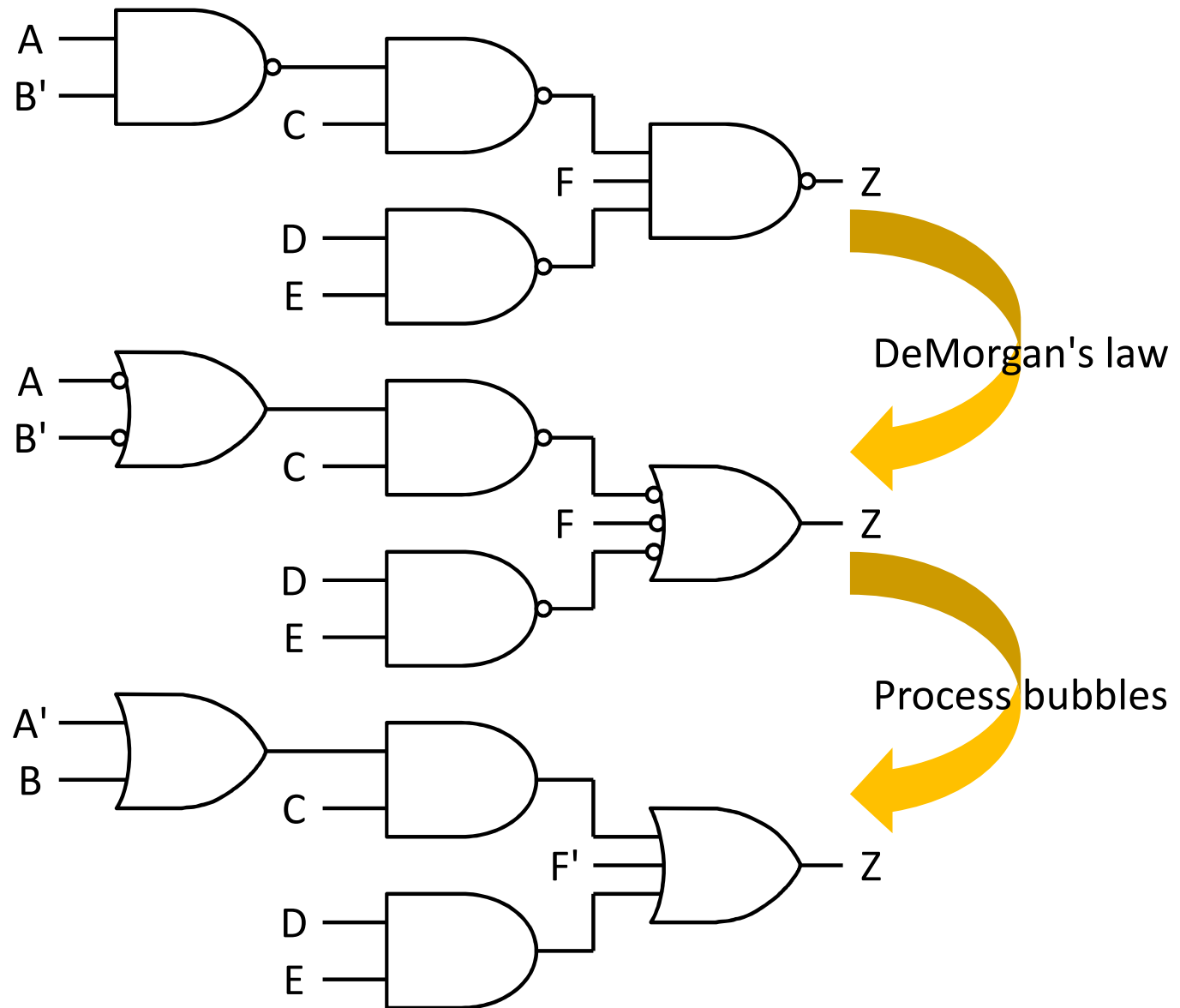



Outline

- ❑ Multi-Level Gate Circuits
- ❑ NAND and NOR Gates
- ❑ Two-Level NAND- and NOR-Gate Circuits
- ❑ Multi-Level NAND- and NOR-Gate Circuits
- ❑ Circuit Conversion Using Alternative Gate Symbols
- ❑ **Design of Two-Level, Multiple-Output Circuits**
- ❑ Multiple-Output NAND and NOR Circuits

Case 1: 4 Inputs and 3 Outputs

□ Example

- $F_1(A,B,C,D) = \sum m(11, 12, 13, 14, 15) = \text{ACD} + \text{AB}$
- $F_2(A,B,C,D) = \sum m(3, 7, 11, 12, 13, 15) = \text{ABC}' + \text{CD} = \text{ABC}' + \text{ACD} + \text{A'CD}$
- $F_3(A,B,C,D) = \sum m(3, 7, 12, 13, 14, 15) = \text{A'CD} + \text{AB}$

 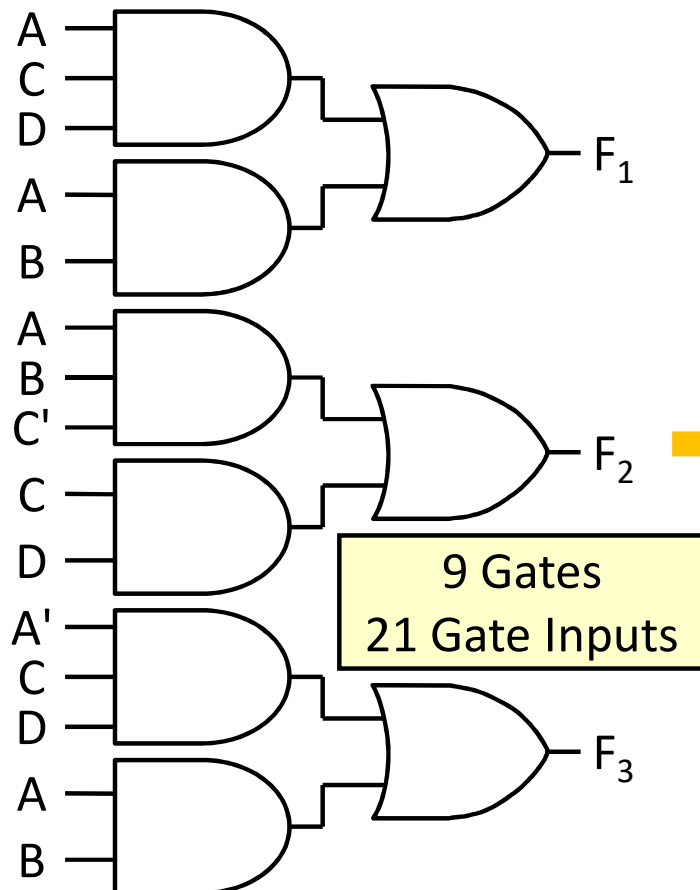

Case 2: 4 Inputs and 3 Outputs (1/2)

□ Example

- $F_1(A,B,C,D) = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15) = BD + B'C + AB'$
- $F_2(A,B,C,D) = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15) = C + A'BD$
- $F_3(A,B,C,D) = \sum m(6, 7, 8, 9, 13, 14, 15) = BC + AB'C' + ABD$ (or $AC'D$)

AB \ CD	00	01	11	10
00				1
01		1	1	1
11	1	1	1	1
10	1			1

AB \ CD	00	01	11	10
00				
01		1		
11	1	1	1	1
10	1	1	1	1

AB \ CD	00	01	11	10
00				1
01			1	1
11		1	1	
10		1	1	

10 Gates
25 Gate Inputs

Case 2: 4 Inputs and 3 Outputs (2/2)

Find common minterms from K-map

- $F_1(A,B,C,D) = \underline{BD} + B'C + \underline{AB'} = \text{ABD} + \text{A'BD} + B'C + \text{AB'C'}$
- $F_2(A,B,C,D) = C + \text{A'BD}$
- $F_3(A,B,C,D) = BC + \text{AB'C'} + \text{ABD}$

AB \ CD	00	01	11	10
00				1
01		1	1	1
11	1	1	1	1
10	1			1

AB \ CD	00	01	11	10
00				
01		1		
11	1	1	1	1
10	1	1	1	1

AB \ CD	00	01	11	10
00				1
01			1	1
11		1	1	
10		1	1	

8 Gates
22 Gate Inputs

Case 3: Essential Prime Implicants

□ Essential for multi-output

- Only check 1's which do not appear in other maps

➤ Example

- $C'D$ and BD' are essential
- ABD and ABC are not

Reduce one gate by sharing ABCD

AB \ CD	00	01	11	10
00				
01	1	1	1	1
11			1	
10				

AB \ CD	00	01	11	10
00		1	1	
01				
11			1	
10		1	1	

AB \ CD	00	01	11	10
00				
01	1	1	1	1
11			1	
10				

AB \ CD	00	01	11	10
00		1	1	
01				
11			1	
10		1	1	

Case 4

- Having more common terms is not always better

8 Gates
26 Gate Inputs

AB \ CD	00	01	11	10
00	1	1		
01		1		
11				
10	1	1	1	

AB \ CD	00	01	11	10
00	1	1	1	
01	1			
11				
10		1	1	

7 Gates
18 Gate Inputs

AB \ CD	00	01	11	10
00	1	1		
01		1		
11				
10	1	1	1	

AB \ CD	00	01	11	10
00	1	1	1	
01	1			
11				
10		1	1	

Summary: 2-Level Multiple-Output Circuits

❑ Cost depends on

- The total # of gates
- The total # of gate inputs

❑ Cost minimization

- A global view may help
 - A minimum SOP for each cannot guarantee minimum cost for all
- Common and essential terms may help
 - Sometimes, we do not need large circles
 - "Essential" is defined in a different way
- Very difficult to find global optimal solution
 - Boolean algebra is very useful in more sophisticated techniques (advanced courses)


Outline

- ❑ Multi-Level Gate Circuits
- ❑ NAND and NOR Gates
- ❑ Two-Level NAND- and NOR-Gate Circuits
- ❑ Multi-Level NAND- and NOR-Gate Circuits
- ❑ Circuit Conversion Using Alternative Gate Symbols
- ❑ Design of Two-Level, Multiple-Output Circuits
- ❑ **Multiple-Output NAND and NOR Circuits**

Multiple-Output NAND & NOR Circuits

□ If all of the output gates are OR/AND gates, direct conversion to a NAND-/NOR-gate circuit is possible

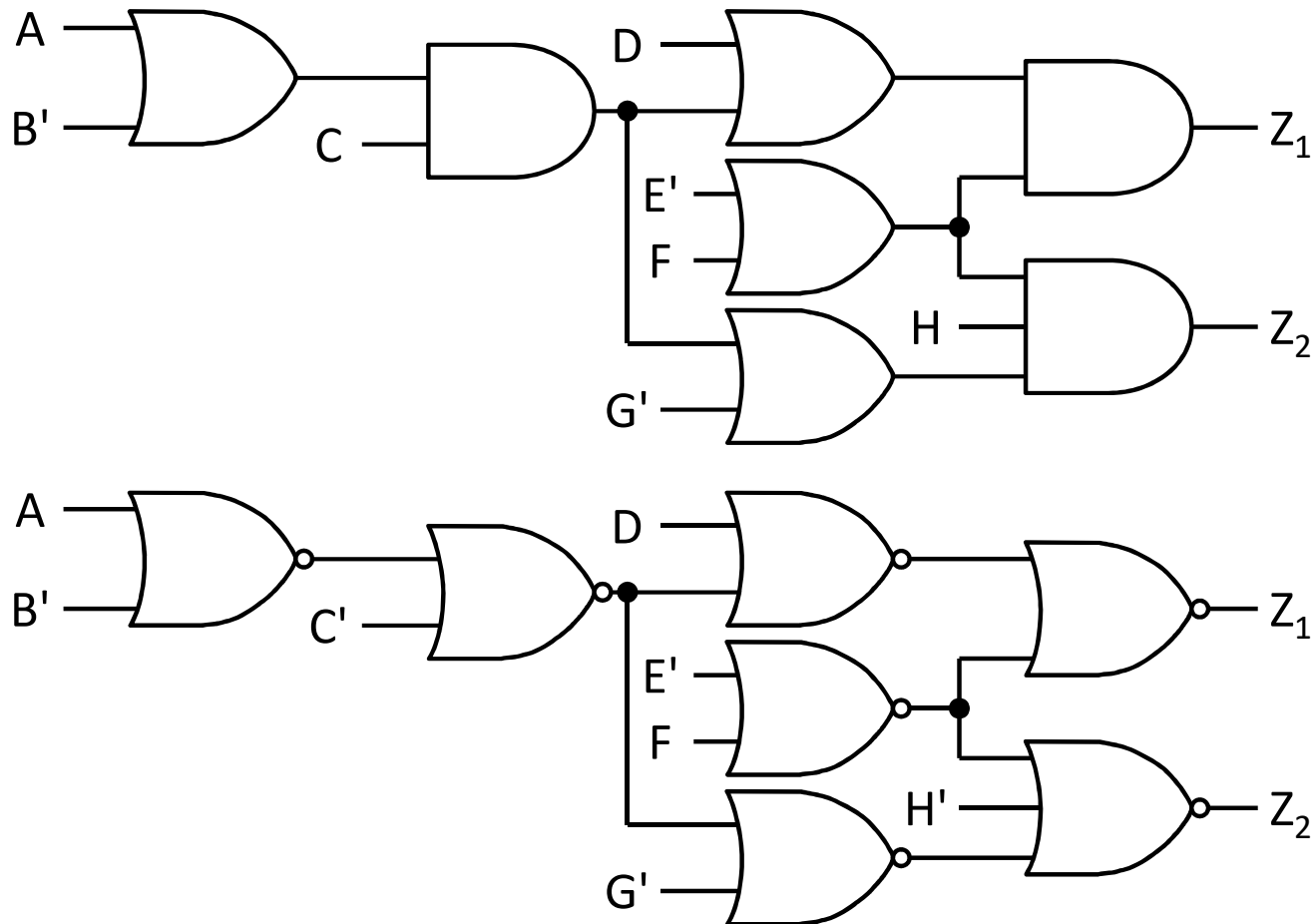➤ Example: $Z_1 = [(A + B')C + D](E' + F)$ and $Z_2 = [(A + B')C + G'](E' + F)H$



Q&A