

# Digital Systems Design and Laboratory

## [ 14. Derivation of State Graphs and Tables ]

Chung-Wei Lin

[cwlin@csie.ntu.edu.tw](mailto:cwlin@csie.ntu.edu.tw)

CSIE Department

National Taiwan University

Spring 2019

# Sequential Logic Design

- ❑ Unit 11: Latches and Flip-Flops
- ❑ Unit 12: Registers and Counters
- ❑ Units 13--15: Finite State Machines
- ❑ Unit 16: Summary
  
- ❑ Designing a sequential circuit
  - Construct a state graph or state table (Unit 14)
  - Simplify it (Unit 15)
  - Derive flip-flop input equations and output equations (Unit 12)

# Outline

- ❑ **Design of a Sequence Detector**
- ❑ Guidelines for Construction of State Graphs
- ❑ Serial Data Code Conversion
- ❑ Alphanumeric State Graph Notation

# "101" Detector (1/5)

❑ Output "1" if detecting "101"


❑ Example

➤ Input X    0 0 1 1 0 1 1 0 0 1 0 1 0 1 0 0

➤ Output Z   0 0 0 0 0 1 0 0 0 0 0 1 0 1 0 0


❑ State graph (Mealy)

 ➤  $S_0$ : initial,  $S_1$ : get "1",  $S_2$ : get "10"



# "101" Detector (2/5)

## State table

 

Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
$S_0$	$S_0$	$S_1$	0	0
$S_1$	$S_2$	$S_1$	0	0
$S_2$	$S_0$	$S_1$	0	1

AB	$A^+B^+$		Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1
11	XX	XX	X	X

# "101" Detector (3/5)

## State maps

AB	A <sup>+</sup> B <sup>+</sup>		Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1
11	XX	XX	X	X



AB \ X	0	1
00	0	0
01	1	0
11	X	X
10	0	0

$$A^+ = X'B$$

AB \ X	0	1
00	0	1
01	0	1
11	X	X
10	0	1

$$B^+ = X$$


AB \ X	0	1
00	0	0
01	0	0
11	X	X
10	0	1

$$Z = XA$$

# "101" Detector (4/5)

## □ Realize it

- $A^+ = X'B$
- $B^+ = X$
- $Z = XA$

 

# "101" Detector (5/5)

## □ Some variants

- Moore machine?
  - One more state
- "010" and "1001" detector
  - A more complicated machine


 


FIGURE 14-10

© Cengage Learning 2014

 

State	Sequence Ends in
S <sub>0</sub>	Reset
S <sub>1</sub>	0 (but not 10)
S <sub>2</sub>	01
S <sub>3</sub>	10
S <sub>4</sub>	1 (but not 01)
S <sub>5</sub>	100



# Outline

- ❑ Design of a Sequence Detector
- ❑ **Guidelines for Construction of State Graphs**
- ❑ Serial Data Code Conversion
- ❑ Alphanumeric State Graph Notation

# Guidelines for Construction of State Graphs


## □ Steps

- Construct sample sequences to help you understand the problem
- Determine under what conditions it should reset
- If only one or two sequences leads to a nonzero output, construct a partial state graph
  - Another way, determine what sequences or groups of sequences must be remembered by the circuit and set up states accordingly
- Each time you add an arrow to the state graph, determine whether it can go to one of the previously defined states or whether a new state must added
- Check your graph to make sure there is one and only one path leaving each state for each combination of values of the input variables
- When your graph is complete, verify it by applying the input sequences formulated in step 1


# Outline

- ❑ Design of a Sequence Detector
- ❑ Guidelines for Construction of State Graphs
- ❑ **Serial Data Code Conversion**
- ❑ Alphanumeric State Graph Notation

# Serial Data Transmission

 

## □ Coding schemes

 

NRZ: Non-Return-to-Zero

0 → 0    1 → 1

NRZI: Non-Return-to-Zero-Inverted

0 → D    1 → D'

RZ: Return-to-Zero

0 → 0    1 → 10

Manchester

0 → 01    1 → 10

# Mealy Machine





## □ Output depends on

- Current state (synchronous)
- Input (maybe asynchronous)



## □ State changes at a falling edge

## □ Fewer states

  
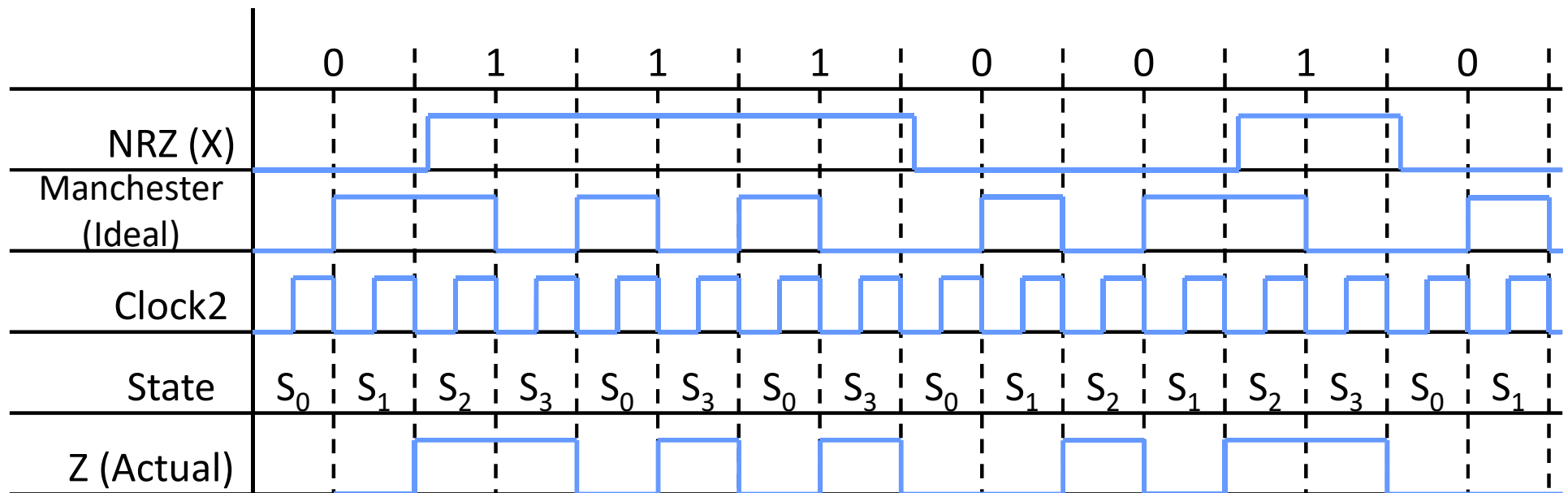 
# Moore Machine

- ❑ Output only depends on
  - Current state (synchronous)
- ❑ State changes at a falling edge
- ❑ More states (in general)
- ❑ 1 clock period delay



# Outline



- ❑ Design of a Sequence Detector
- ❑ Guidelines for Construction of State Graphs
- ❑ Serial Data Code Conversion
- ❑ **Alphanumeric State Graph Notation**

# Alphanumeric State Graph Notation

- When a sequential circuit has several inputs, label the state graph arcs with alphanumeric input variable names instead of 0's and 1's

➤ Example

  - 2 inputs: F for "forward" and R for "reverse"







# Completely Specified State Graph
  
## □ Properties

- **OR** together all input labels on arcs emanating from a state, the result can reduce to 1
  - Cover all conditions:  $F + F'R + F'R' = F + F' = 1$
- **AND** together any pair of input labels on arcs emanating from a state, the result can reduce to 0
  - Only one arc is valid:  $F \cdot F'R = 0$ ,  $F \cdot F'R' = 0$ ,  $F'R \cdot F'R' = 0$



# Q&A