

Digital Systems Design and Laboratory

[11. Latches and Flip-Flops]

Chung-Wei Lin

cwlin@csie.ntu.edu.tw

CSIE Department

National Taiwan University

Spring 2019

We would like to thank Prof. Hui-Ru Jiang (NTU) for contributing the lecture material


Recap: Two Types of Switching Circuits

□ Combinational circuits (memoryless)

- Outputs depend only on present inputs

□ Sequential circuits


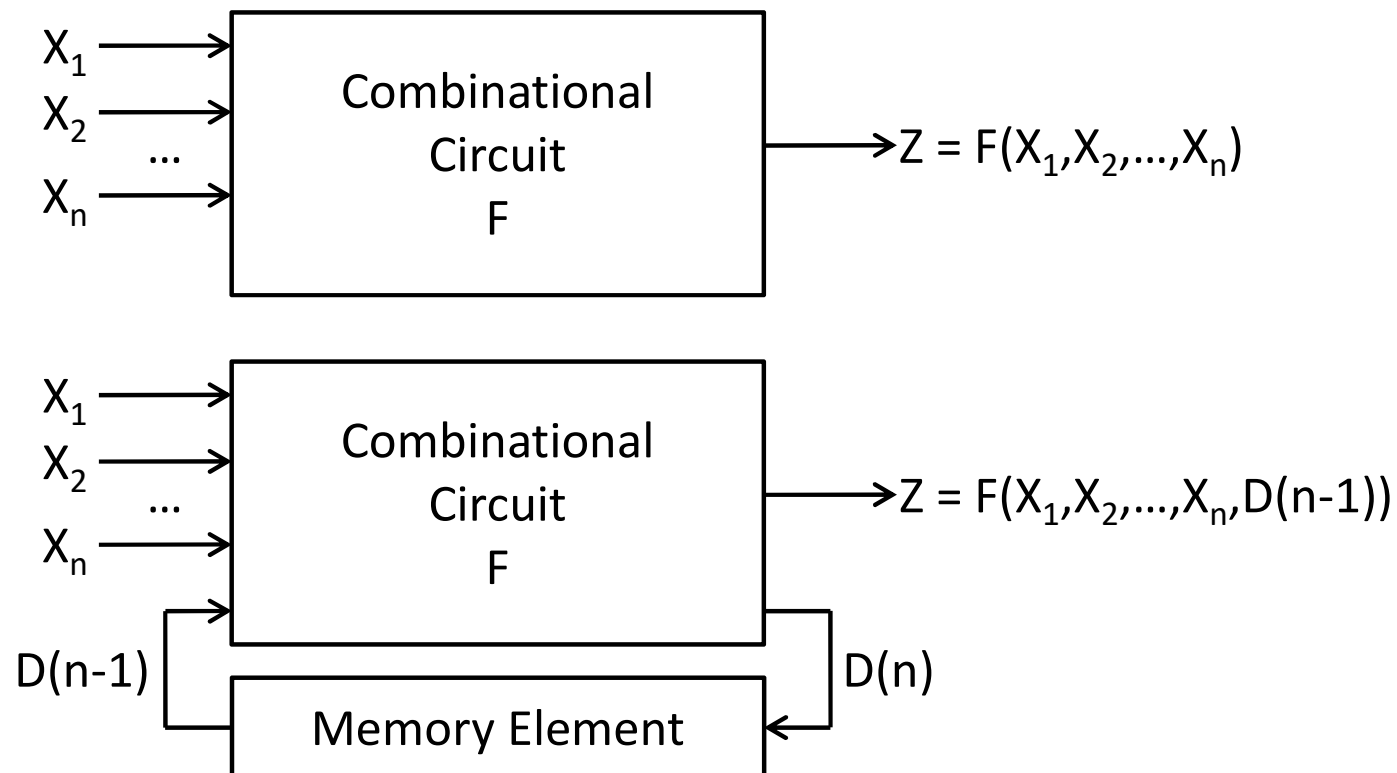
- Outputs depend on both present and past inputs
- In general, sequential circuits = combinational circuits + memory





How to Remember the Past?


□ Feedback

  - The output of one of the gates is connected back into the input of another gate in the circuit so as to form a closed loop
- Example: inverter with feedback
 - Q: How fast does the circuit oscillate?
 - A: Determined by the propagation delay of the inverter



  - Example: a feedback loop with two inverters
 - Two stable states
 - Latch: basic memory unit (store 1 bit)






 


Outline

☒ Set-Reset Latch


- ☐ Gated D Latch
- ☐ Edge-Triggered D Flip-Flop
- ☐ S-R Flip-Flop
- ☐ J-K Flip-Flop
- ☐ T Flip-Flop
- ☐ Flip-Flops with Additional Inputs

Set-Reset (S-R) Latch (1/2)

    


Set-Reset (S-R) Latch (2/2)

❑ Cross-coupled form

 

❑ $S = R = 1$ not allowed!

 - Note that the outputs are Q and Q'
- An oscillation scenario
 - Both S and R: $1 \rightarrow 0$
 - Both P and Q: $0 \rightarrow 1 \rightarrow 0 \rightarrow 1$
 - If the gate delays are equal



Next-State (Characteristic) Equation

□ Operation



S	R	Q	Q ⁺	
0	0	0	0	Unchanged
0	0	1	1	
0	1	0	0	Reset to 0
0	1	1	0	
1	0	0	1	Set to 1
1	0	1	1	
1	1	0	X	Inputs Not Allowed
1	1	1	X	

RQ \ S		0	1
		00	01
00		0	1
01		1	1
11		0	X
10		0	X

$$Q^+ = S + R'Q$$



Application: Switch Debouncing

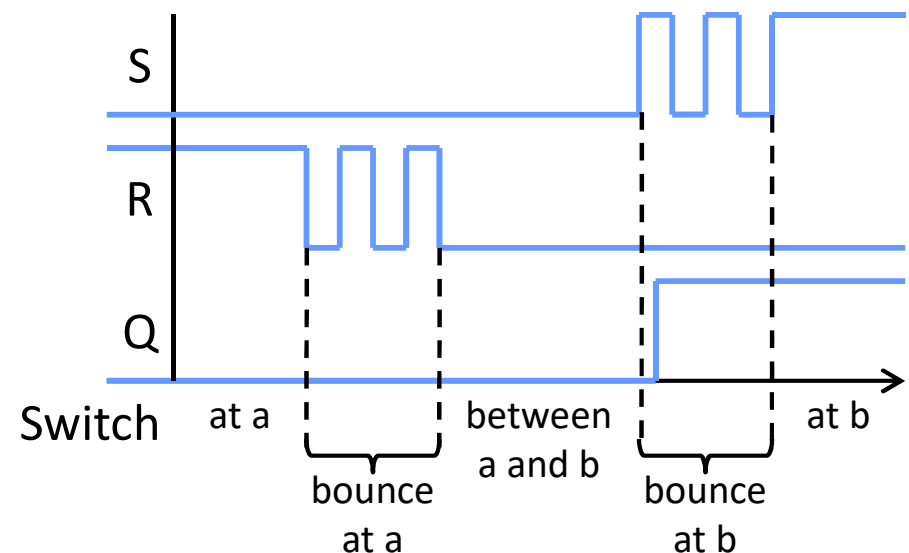 - ❑ When a mechanical switch is opened or closed, switch contacts tend to vibrate before settling down
- ❑ Debounce with S-R latch
 - When the switch is flipped from a to b...
 - Work only with a "double throw" switch
 - Double throw: switch between two contacts
 - Single throw: switch between one contact and open




Alternative Form with NAND-Gates

  □ \bar{S} - \bar{R} latch: active-low inputs for S & R





\bar{S}	\bar{R}	Q	Q ⁺	
1	1	0	0	Unchanged
1	1	1	1	
1	0	0	0	Reset to 0
1	0	1	0	
0	1	0	1	Set to 1
0	1	1	1	
0	0	0	X	Inputs Not Allowed
0	0	1	X	

 

Outline

- ☐ Set-Reset Latch
- ☒ **Gated D Latch**
- ☐ Edge-Triggered D Flip-Flop
- ☐ S-R Flip-Flop
- ☐ J-K Flip-Flop
- ☐ T Flip-Flop
- ☐ Flip-Flops with Additional Inputs

Gated D Latch

  


G	D	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Unchanged
 $Q^+ = Q$

$Q^+ = D$

		G	
		0	1
DQ	00	0	0
	01	1	0
	11	1	1
	10	0	1

$$Q^+ = G'Q + GD$$

 


Outline

- ☐ Set-Reset Latch
- ☐ Gated D Latch
- ☒ **Edge-Triggered D Flip-Flop**
- ☐ S-R Flip-Flop
- ☐ J-K Flip-Flop
- ☐ T Flip-Flop
- ☐ Flip-Flops with Additional Inputs


Edge-Triggered D Flip-Flops (1/2)

□ Output changes are aligned with clock edges

 - Positive (rising-edge) trigger
- Negative (falling-edge) trigger




 - Next-state (characteristic) equation: $Q^+ = D$
- Timing diagram for a falling-edge triggered D flip-flop




Edge-Triggered D Flip-Flops (2/2)

 - Construct a rising-edge triggered D flip-flop from 2 gated D latches



- Time diagram

 

Setup Times and Hold Times

□ Setup time

- The amount of time that D must be stable before the active edge


□ Hold time


- The amount of time that D must hold the same value after the active edge

FIGURE 11-20

Setup and Hold Times for an Edge-Triggered D Flip-Flop

© Cengage Learning 2014

 

 


Outline

- ☐ Set-Reset Latch
- ☐ Gated D Latch
- ☐ Edge-Triggered D Flip-Flop
- ☒ **S-R Flip-Flop**
- ☐ J-K Flip-Flop
- ☐ T Flip-Flop
- ☐ Flip-Flops with Additional Inputs


S-R Flip-Flop


- ❑ Output changes at rising edges
- ❑ Construct from 2 latches

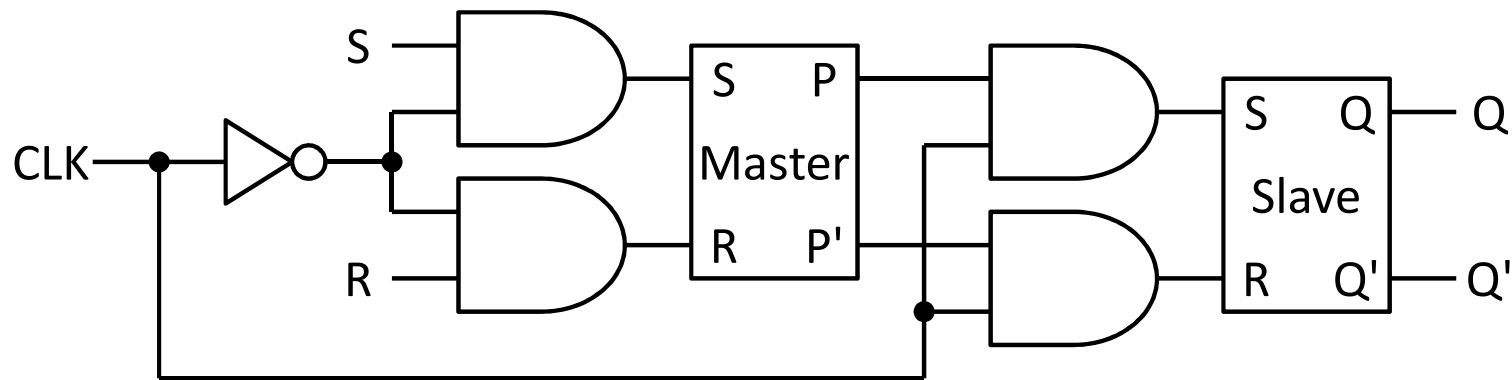Not desired --- should only allow the S and R inputs to change while the clock is high



S	R	Operation
0	0	No state change
0	1	Reset Q to 0 (after active CLK edge)
1	0	Set Q to 1 (after active CLK edge)
1	1	Not allowed

 

 

Outline


- ☐ Set-Reset Latch
- ☐ Gated D Latch
- ☐ Edge-Triggered D Flip-Flop
- ☐ S-R Flip-Flop
- ☒ **J-K Flip-Flop**
- ☐ T Flip-Flop
- ☐ Flip-Flops with Additional Inputs

J-K Flip-Flop

Extension of S-R flip-flop


➤ J: jump to 1


➤ K: clear to 0

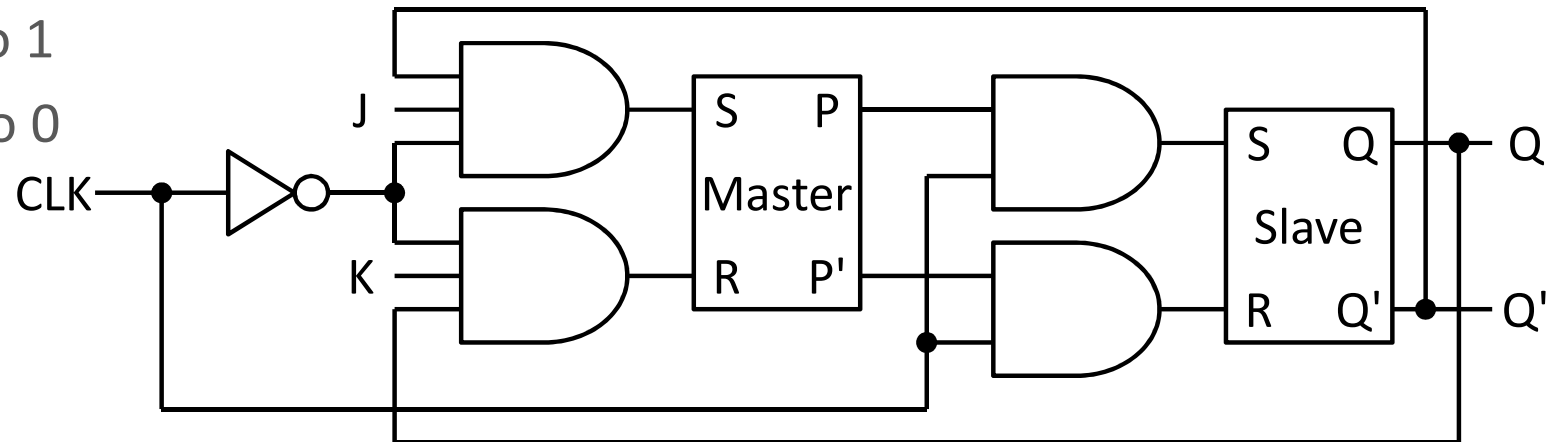

J	K	Q	Q ⁺	
0	0	0	0	Unchanged
0	0	1	1	
0	1	0	0	Clear to 0
0	1	1	0	
1	0	0	1	Jump to 1
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

$$Q^+ = JQ' + K'Q$$

 

 

Outline


- ☐ Set-Reset Latch
- ☐ Gated D Latch
- ☐ Edge-Triggered D Flip-Flop
- ☐ S-R Flip-Flop
- ☐ J-K Flip-Flop
- ☒ **T Flip-Flop**
- ☐ Flip-Flops with Additional Inputs

T Flip-Flop



□ T: toggle

T	Q	Q ⁺	
0	0	0	Unchanged
0	1	1	
1	0	1	Toggle
1	1	0	

$$Q^+ = TQ' + T'Q$$

 

□ Implementations

  


Outline

- ☐ Set-Reset Latch
- ☐ Gated D Latch
- ☐ Edge-Triggered D Flip-Flop
- ☐ S-R Flip-Flop
- ☐ J-K Flip-Flop
- ☐ T Flip-Flop
- ☐ **Flip-Flops with Additional Inputs**

Flip-Flops with Additional Inputs

❑ Set a flip-flop to an initial state independent of the clock


➤ Example: asynchronous Clear and Preset

 

Ck	D	PreN	ClrN	Q ⁺
X	X	0	0	Not Allowed
X	X	0	1	1
X	X	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0, 1, ↓	X	1	1	Q (Unchange)

❑ Let a flip-flop hold existing data even though the data input may be changing

 ➤ Gated clock: gate the clock by Clock Enable (CE)



Summary

Type	Q^+
S-R Latch	$S + R'Q$
Gated D Latch	$G'Q + GD$
D Flip-Flop	D
S-R Flip-Flop	$S + R'Q$
J-K Flip-Flop	$JQ' + K'Q$
T Flip-Flop	$TQ' + T'Q$
D-CE Flip-Flop	$D(CE) + Q(CE)'$

Q&A

Announcement (0429)

□ Homework 3

- Due at noon on May 6
- TA provided some detailed explanation on NTU COOL

□ Guest talks next week (Please come!)

- 1:20--1:50pm: Synopsys
- 2:20--2:40pm: Dean Yao-Wen Chang
- May 13: MediaTek, Prof. Hui-Ru Jiang
- May 20: Prof. Jie-Hone Jiang