

# Digital Systems Design and Laboratory

## [ 12. Registers and Counters ]

Chung-Wei Lin

[cwlin@csie.ntu.edu.tw](mailto:cwlin@csie.ntu.edu.tw)

CSIE Department

National Taiwan University

Spring 2019

# Sequential Logic Design

## ❑ Unit 11: Latches and Flip-Flops

- Basic unit

## ❑ Unit 12: Registers and Counters

- Simple sequential circuit

## ❑ Units 13--15: Finite State Machines

- Complex sequential circuit

## ❑ Unit 16: Summary

- Put it all together

# Outline

## ☐ **Registers and Register Transfers**

☐ Shift Registers


☐ Design of Binary Counters

☐ Counters for Other Sequence

☐ Counter Design Using S-R and J-K Flip-Flops

☐ Derivation of Flip-Flop Input Equations

# Registers (1/2)

 


❑ Register: a group of D flip-flops with a common clock

❑ Example


➤ 4-bit D flip-flop registers with Data, Load, Clear (ClrN), Clock (Clk)

❑ First Implementation: gated clock

 ➤ When Load = 1, load data at D to Q at Clk falling



# Registers (2/2)

 


❑ Register: a group of D flip-flops with a common clock

❑ Example

➤ 4-bit D flip-flop registers with Data, Load, Clear (ClrN), Clock (Clk)

❑ Second implementation: clock enable

 
➤ When Load = 1, load data at D to Q at Clk falling



# Data Transfer between Registers

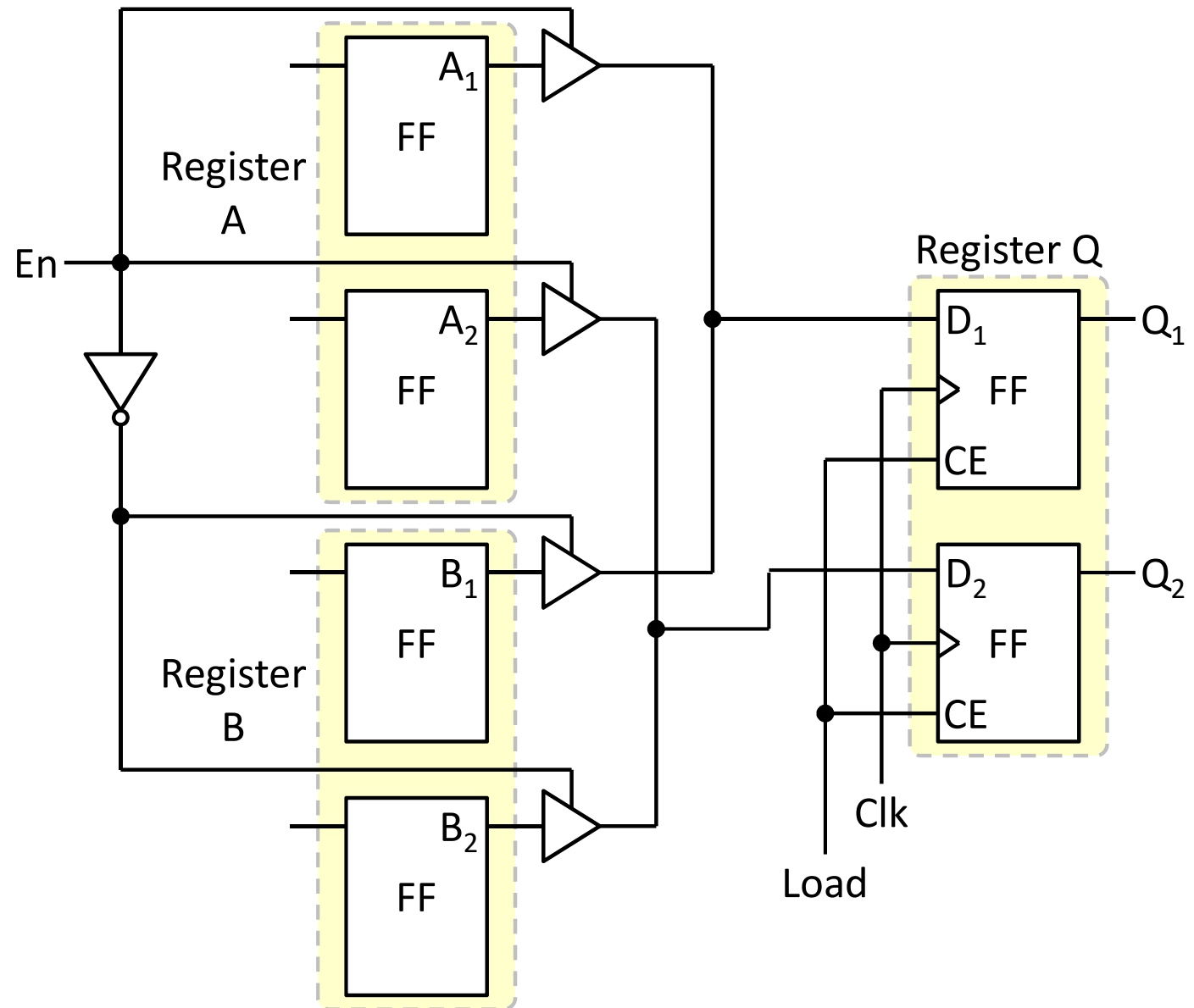
## 2-to-1 MUX

- If  $En = 1$ ,  $Q = A$
- If  $En = 0$ ,  $Q = B$




# 8-Bit Register with Tri-State Output (1/2)

## □ Symbol

 


## □ Logic diagram

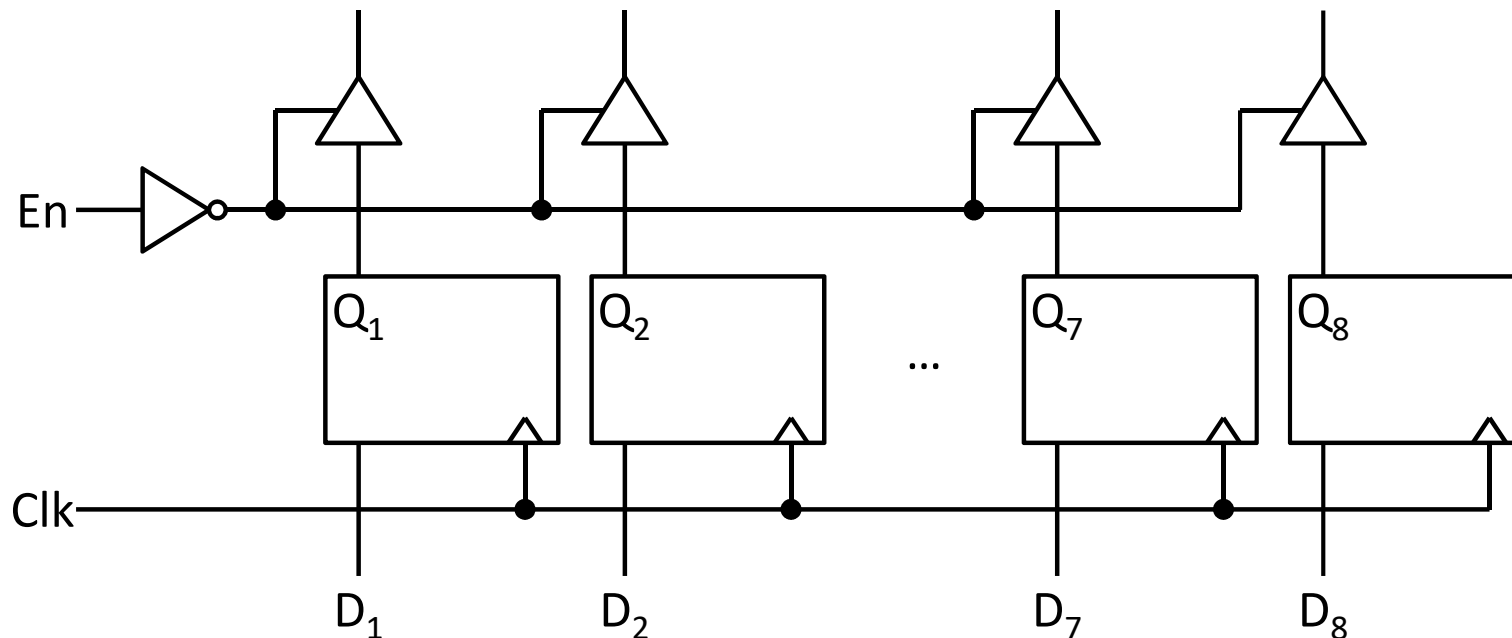

# 8-Bit Register with Tri-State Output (2/2)

## □ Data transfer

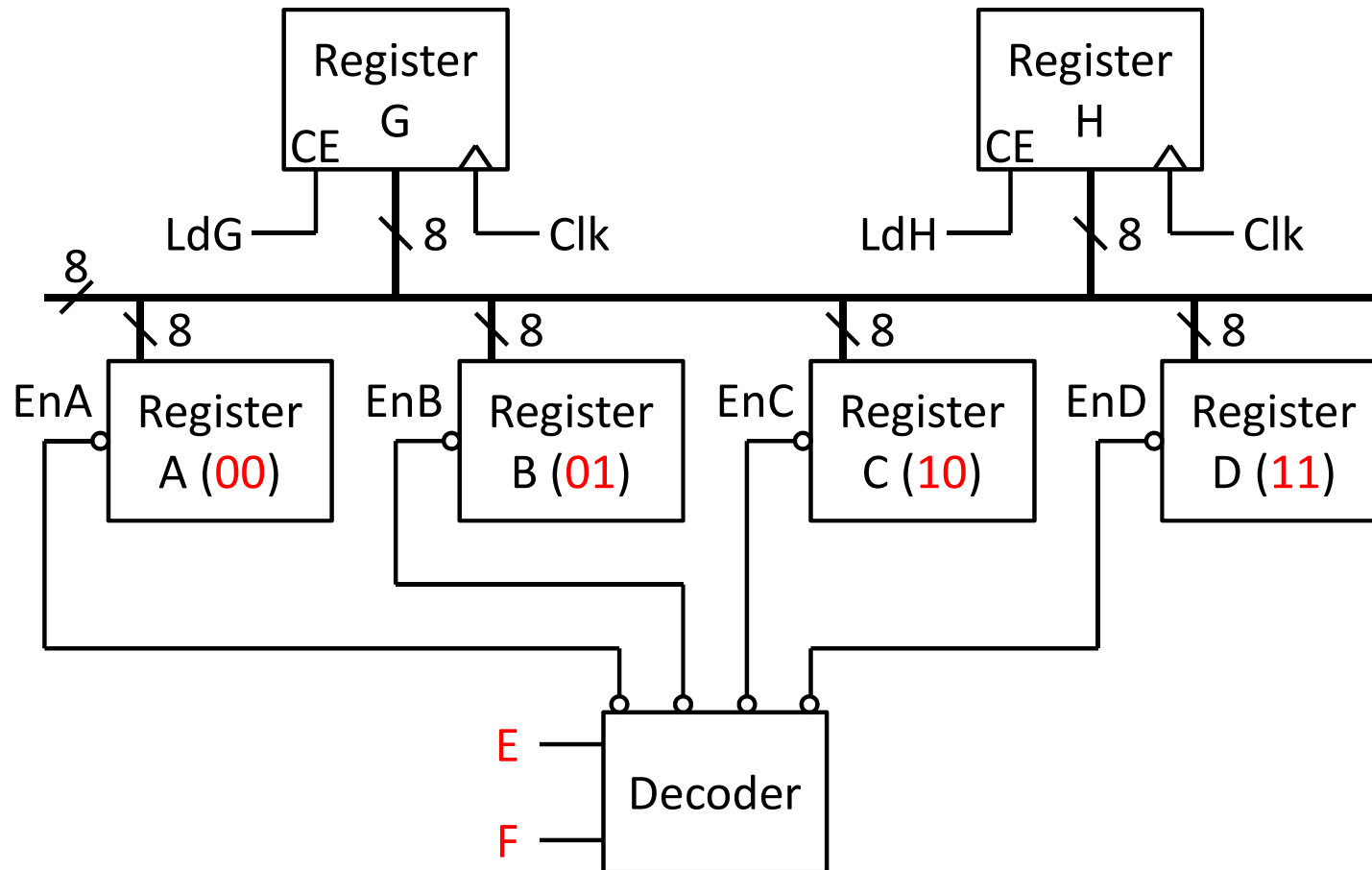




# Outline

- ❑ Registers and Register Transfers
- ❑ **Shift Registers**
- ❑ Design of Binary Counters
- ❑ Counters for Other Sequence
- ❑ Counter Design Using S-R and J-K Flip-Flops
- ❑ Derivation of Flip-Flop Input Equations


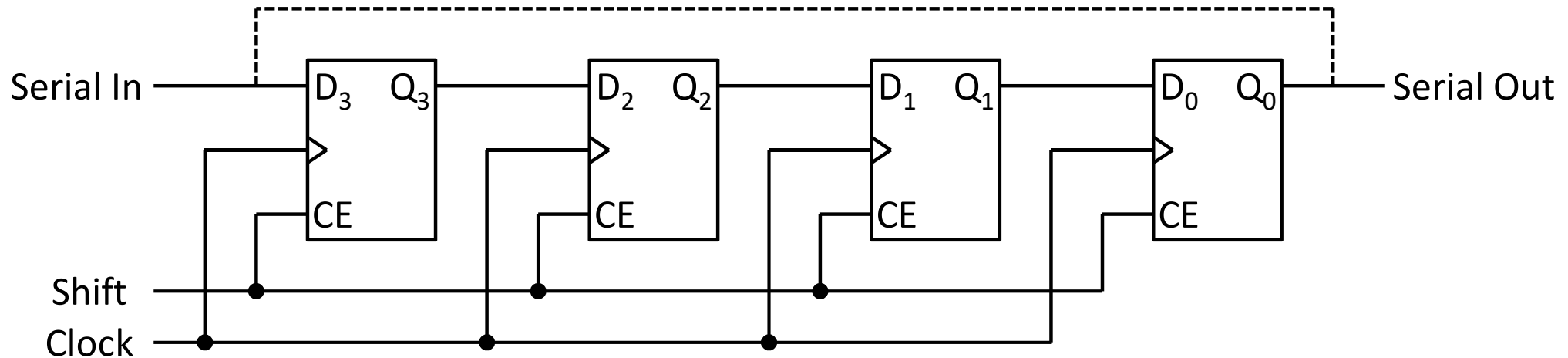
# Shift Registers (1/2)

- ❑ Shift register: a group of flip-flops where binary data can be stored and shifted left or right when a shift signal is applied
- ❑ Example: 4-bit right-shift register



# Shift Registers (2/2)
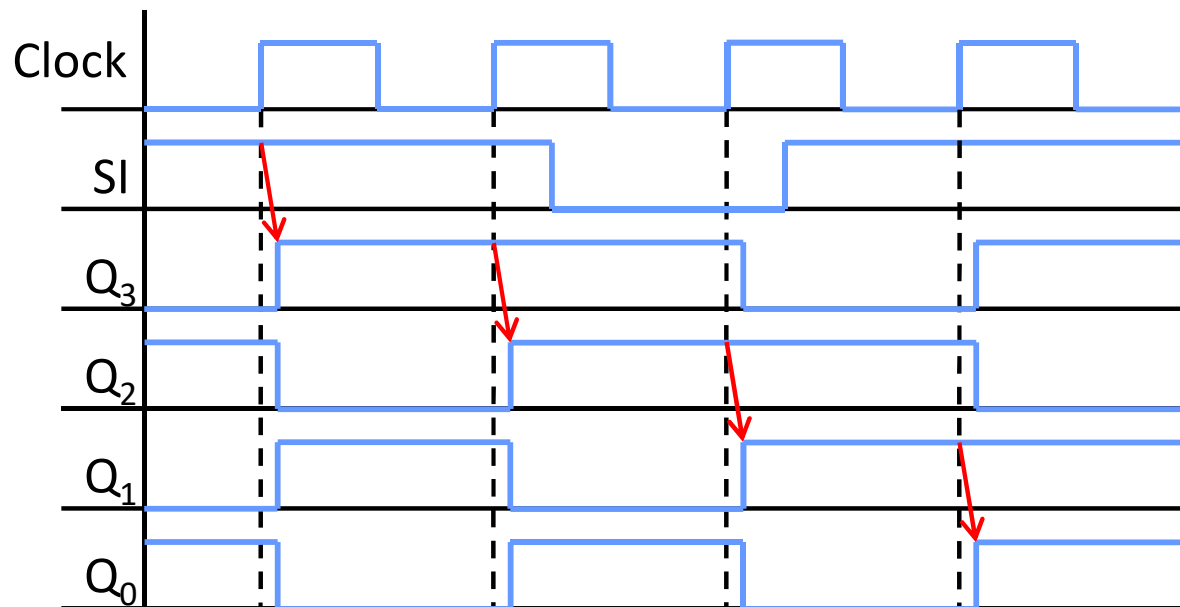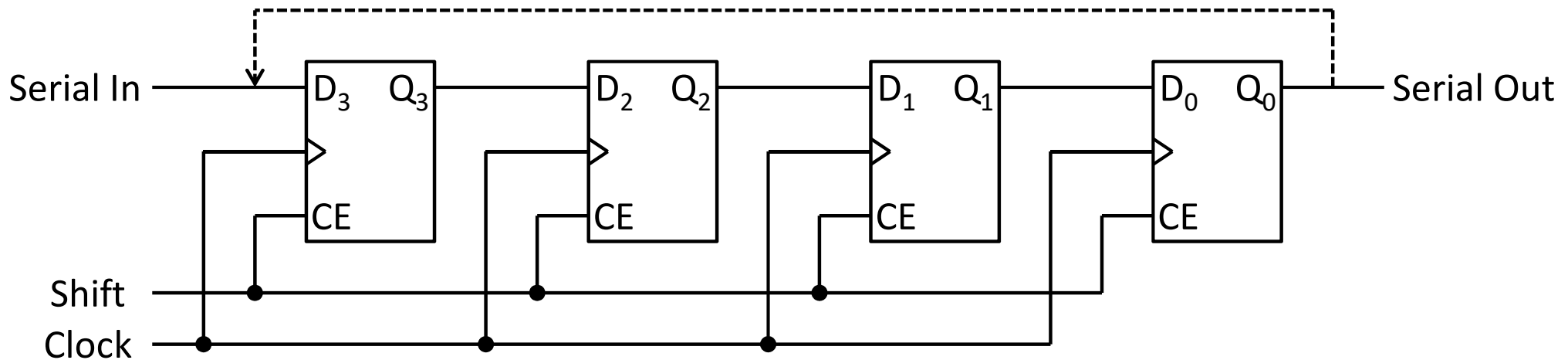
## □ Timing diagram of a 4-bit right-shift register



Initial Q<sub>3</sub>Q<sub>2</sub>Q<sub>1</sub>Q<sub>0</sub> = 0101

SI = 1, 1, 0, 1

Q<sub>3</sub>Q<sub>2</sub>Q<sub>1</sub>Q<sub>0</sub> = 0101

**1**010

**11**01

**011**0


**1011**

# N-bit Serial-In Serial-Out Shift Registers

❑ Take  $(n-1)$  cycles to output data

➤ SI: Serial In


➤ SO: Serial Out

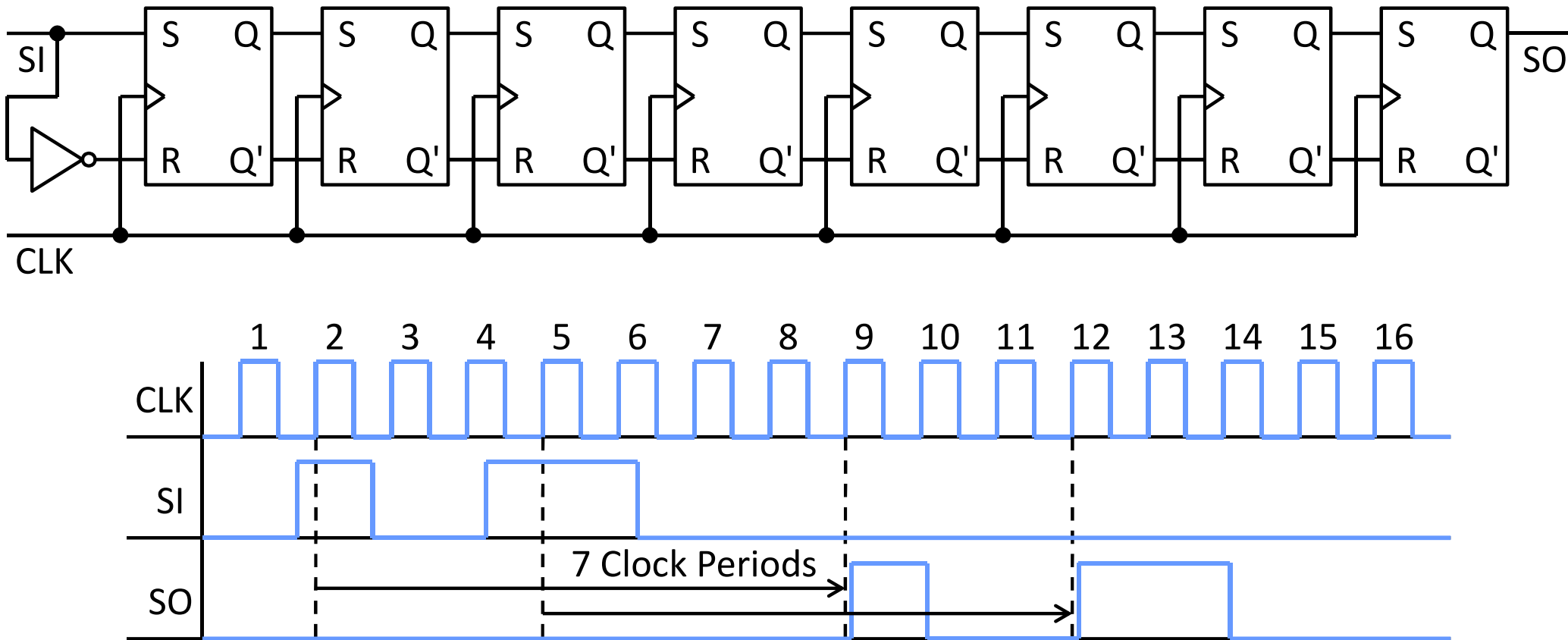

# Parallel-In Parallel-Out Right Shift Register (1/2)
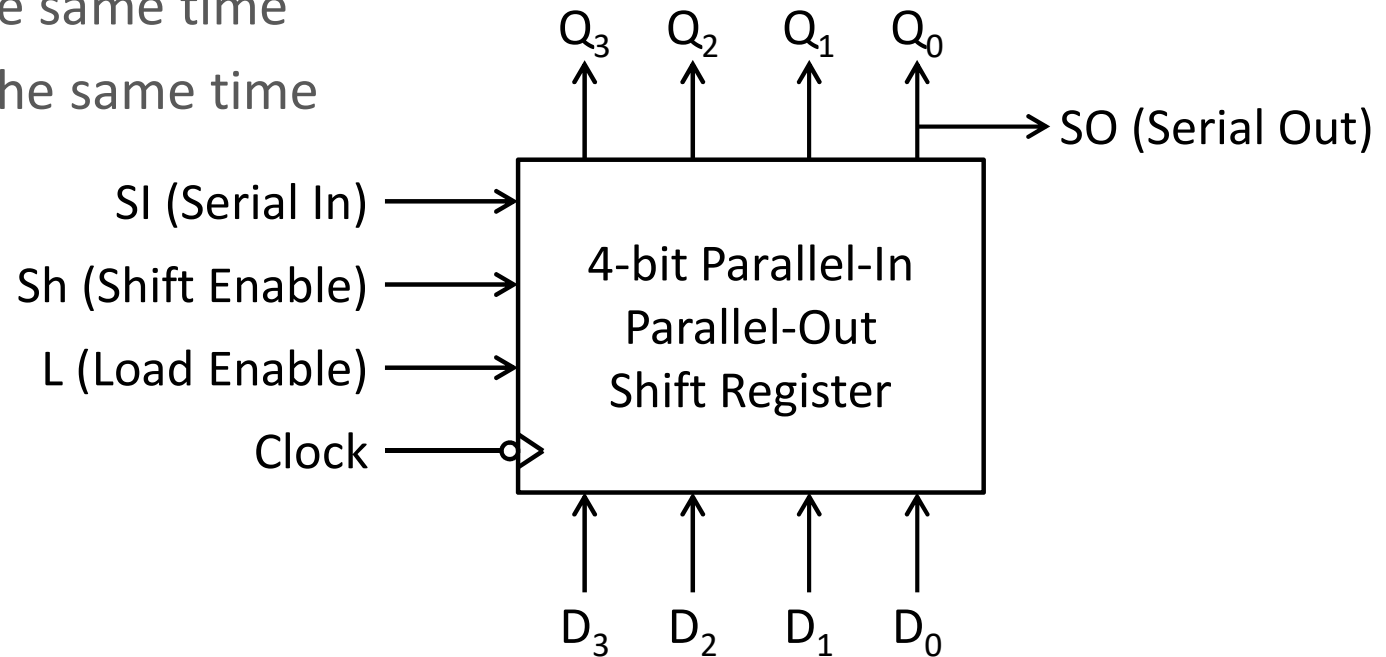
## □ Parallel-in parallel-out (PIPO)


- Load all data at the same time
- Read out data at the same time



Sh (Shift)	L (Load)	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	Action
0	0	$Q_3$	$Q_2$	$Q_1$	$Q_0$	No Change
0	1	$D_3$	$D_2$	$D_1$	$D_0$	Load
1	X	SI	$Q_3$	$Q_2$	$Q_1$	Right Shift

# Parallel-In Parallel-Out Right Shift Register (2/2)


□ Implement using flip-flops and MUXes

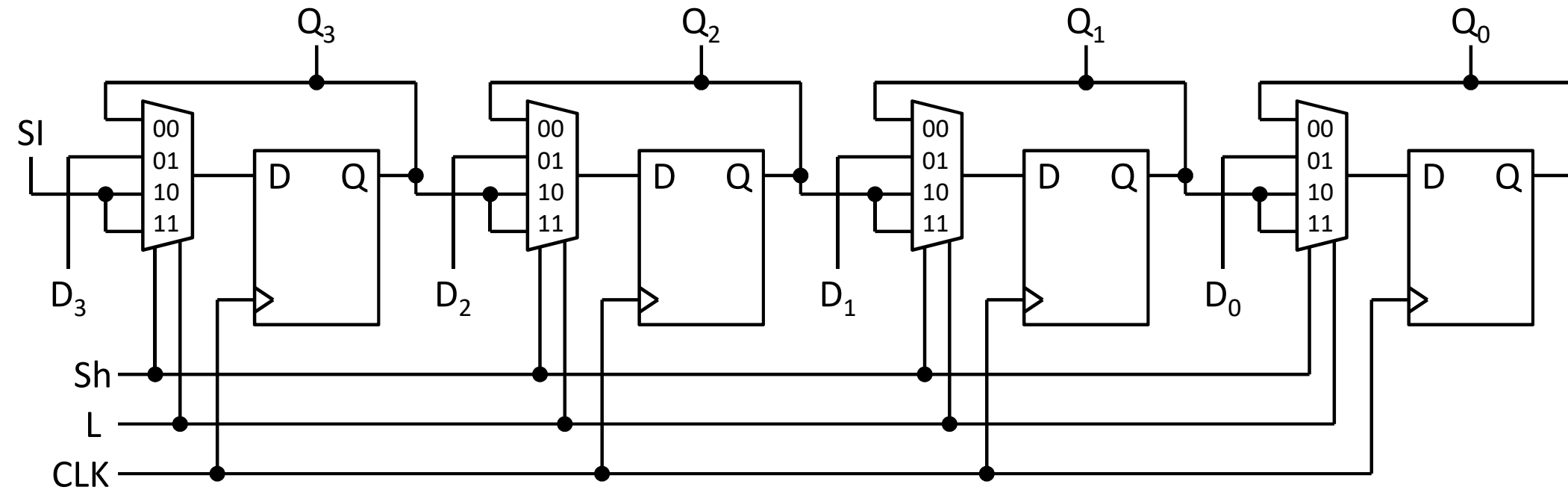


# Shift Register with Inverted Feedback
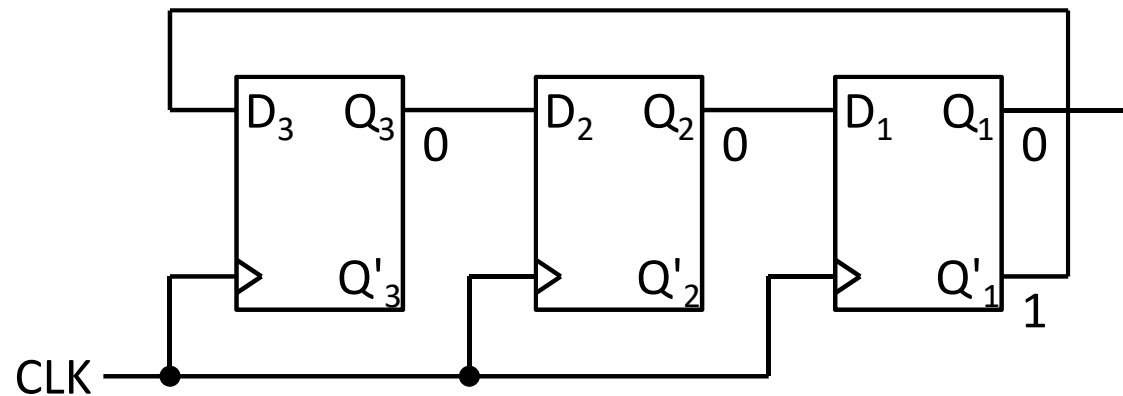
## □ Johnson counter: a shift register with inverted feedback

➤ Counter: a circuit that cycles through a fixed sequence of states



## □ State graph

 

# Outline


- ☐ Registers and Register Transfers
- ☐ Shift Registers
- ☒ **Design of Binary Counters**
- ☐ Counters for Other Sequence
- ☐ Counter Design Using S-R and J-K Flip-Flops
- ☐ Derivation of Flip-Flop Input Equations



# Counting 0--7 (1/2)

- ❑ Synchronous counter: flip-flops are synchronized by a clock
- ❑ First implementation: T flip-flops


Present State			Next State			Flip-Flop Inputs (By Observation)		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

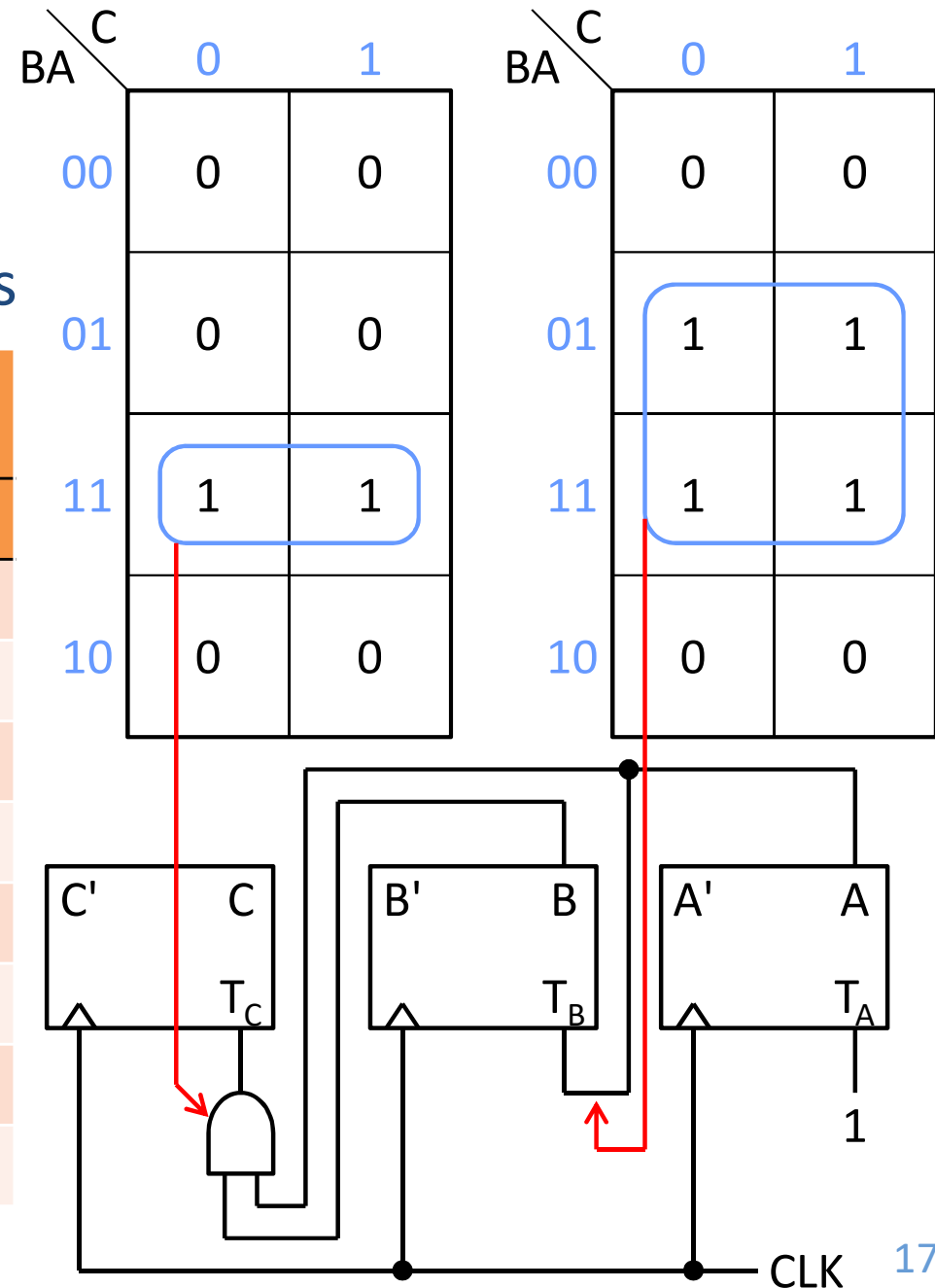

# Counting 0--7 (2/2)
 
## ❑ Second implementation: D flip-flops

- $D_A = A^+ = A'$
- $D_B = B^+ = BA' + B'A = B \oplus A$ 
  - B changes when  $A = 1$
- $D_C = C^+ = C'BA + CB' + CA' = C \oplus BA$ 
  - C changes when  $A = B = 1$




Present State			Next State		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

# Up-Down Counter
 
## □ U and D control "up" and "down"

- Do not allow  $U = D = 1$
- $D_A = A^+ = A \oplus (U + D)$
- $D_B = B^+ = B \oplus (UA + DA')$
- $D_C = C^+ = C \oplus (UBA + DB'A')$




CBA	$C^+B^+A^+$	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

# Outline

- ☐ Registers and Register Transfers
- ☐ Shift Registers
- ☐ Design of Binary Counters
- ☒ **Counters for Other Sequence**
- ☐ Counter Design Using S-R and J-K Flip-Flops
- ☐ Derivation of Flip-Flop Input Equations
 
# State Diagram of Counter

❑ What if the sequence is not in straight binary order?



Present State			Next State		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

# K-Map Derivation

□ Next states

C		0	1
BA	00	1	1
	01	X	X
	11	0	0
	10	0	X

$C^+$

C		0	1
BA	00	0	1
	01	X	X
	11	0	1
	10	1	X

$B^+$

C		0	1
BA	00	0	1
	01	X	X
	11	0	0
	10	1	X

$A^+$

C	B	A	$C^+$	$B^+$	$A^+$
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

# Implementation: T Flip-Flops (1/2)

□ T inputs:  $T = Q \oplus Q^+$

		C	
BA		0	1
00	1	0	
01	X	X	
11	0	1	
10	0	X	

$$T_C = C'B' + CB$$

		C	
BA		0	1
00	0	1	
01	X	X	
11	1	0	
10	0	X	


$$T_B = C'A + CB'$$

		C	
BA		0	1
00	0	1	
01	X	X	
11	1	1	
10	1	X	

$$T_A = C + B$$

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

## Implementation: T Flip-Flops (2/2)

 




# Don't Care States
 
## ❑ If flip-flops are initially set to CBA = 001

- Tracking signals through the network shows that  $T_C = T_B = 1$  and  $T_A = 0$ , so the state changes to 111



## ❑ When the power is turned on, the initial states of all flip-flops are unpredictable!!

- Don't care states should be checked to make sure that they eventually lead into the main counting sequence
- Or use power-up reset

# Implementation: D Flip-Flops (1/2)

□ Next states

		C	
		0	1
BA	00	1	1
	01	X	X
	11	0	0
	10	0	X

$$D_C = B'$$

		C	
		0	1
BA	00	0	1
	01	X	X
	11	0	1
	10	1	X


$$D_B = C + BA'$$

		C	
		0	1
BA	00	0	1
	01	X	X
	11	0	0
	10	1	X

$$D_A = CA' + BA'$$

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

# Implementation: D Flip-Flops (2/2)

 

# Outline

- ☐ Registers and Register Transfers
- ☐ Shift Registers
- ☐ Design of Binary Counters
- ☐ Counters for Other Sequence
- ☐ **Counter Design Using S-R and J-K Flip-Flops**
- ☐ Derivation of Flip-Flop Input Equations

# Recap: S-R Flip-Flops

## □ What is the relation between S, R and Q, Q<sup>+</sup>?


➤ We do it reversely from Q and Q<sup>+</sup> to S and R

S	R	Q	Q <sup>+</sup>		Q	Q <sup>+</sup>	S	R		Q	Q <sup>+</sup>	S	R
0	0	0	0	} Unchanged	0	0	0	0	} Unchanged	0	0	0	X
0	0	1	1		0	0	0	1		0	0	0	X
0	1	0	0	} Reset to 0	0	1	1	0	} Reset to 0	0	1	1	0
0	1	1	0		0	1	1	0		0	1	1	0
1	0	0	1	} Set to 1	1	0	0	1	} Set to 1	1	0	0	1
1	0	1	1		1	0	0	1		1	0	0	1
1	1	0	X	} Inputs Not Allowed	1	1	0	0	} Inputs Not Allowed	1	1	X	0
1	1	1	X		1	1	1	0		1	1	X	0

Excitation Table
 
# Using S-R Flip-Flops (1/2)

- Derive S-R flip-flop inputs from the excitation table



Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0



C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	S <sub>C</sub>	R <sub>C</sub>	S <sub>B</sub>	R <sub>B</sub>	S <sub>A</sub>	R <sub>A</sub>
0	0	0	1	0	0	1	0	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	0	0	0	0	X	0	1	0	1
1	0	0	1	1	1	X	0	1	0	1	0
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	0	1	X	0	0	1

By Karnaugh maps

$$S_C = B', R_C = A, S_B = C, R_B = C'A, S_A = CA' + BA', R_A = A$$

# Using S-R Flip-Flops (2/2)

- Alternative: derive S-R flip-flop inputs with K-maps (faster?)

Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

		C	
		0	1
BA	00	1	1
	01	X	X
	11	0	0
	10	0	X
		$C^+$	



		C	
		0	1
BA	00	1	X
	01	X	X
	11	0	0
	10	0	X
		$S_C = B'$	

		C	
		0	1
BA	00	0	0
	01	X	X
	11	X	1
	10	X	X
		$R_C = A$	

# Recap: J-K Flip-Flops

## □ What is the relation between J, K and Q, Q<sup>+</sup>?


➤ We do it reversely from Q and Q<sup>+</sup> to J and K

J	K	Q	Q <sup>+</sup>		Q	Q <sup>+</sup>	J	K		Q	Q <sup>+</sup>	J	K
0	0	0	0	} Unchanged	0	0	0	0	} Unchanged	0	0	0	X
0	0	1	1		0	0	0	1		0	0	0	X
0	1	0	0	} Reset to 0	0	1	1	0	} Reset to 0	0	1	1	X
0	1	1	0		0	1	1	1		0	1	1	X
1	0	0	1	} Set to 1	1	0	0	1	} Set to 1	1	0	X	1
1	0	1	1		1	0	1	1		1	0	X	1
1	1	0	1	} Toggle	1	1	0	0	} Toggle	1	1	X	0
1	1	1	0		1	1	1	0		1	1	X	0


 
# Using J-K Flip-Flops

- Derive J-K flip-flop inputs from the excitation table



Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0




C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	J <sub>C</sub>	K <sub>C</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	X	1	X	0	X	1

By Karnaugh maps


$$J_C = B', K_C = A, J_B = C, K_B = C'A, J_A = C + B, K_A = 1$$

# Implementation

## □ S-R flip-flops

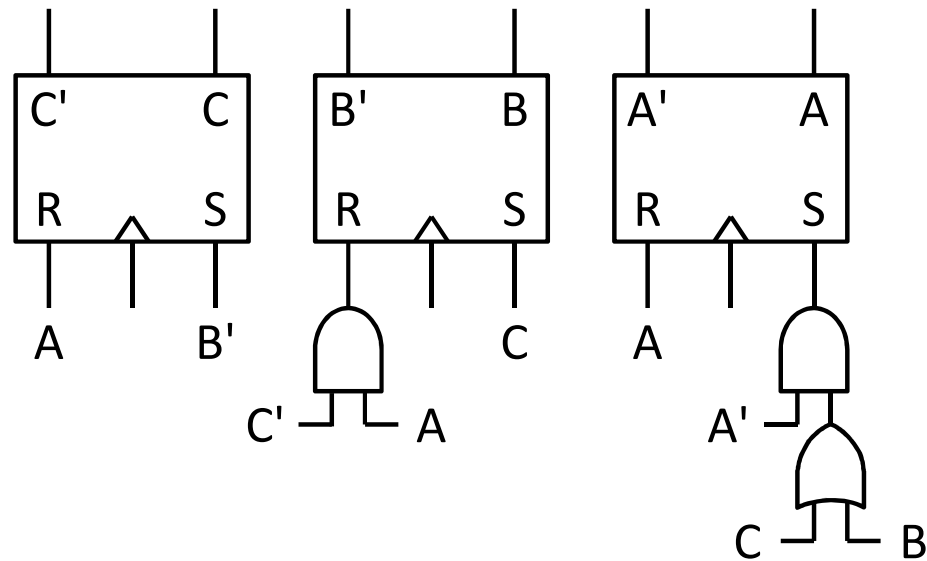

## □ J-K flip-flops

 

# Outline

- ❑ Registers and Register Transfers
- ❑ Shift Registers
- ❑ Design of Binary Counters
- ❑ Counters for Other Sequence
- ❑ Counter Design Using S-R and J-K Flip-Flops
- ❑ **Derivation of Flip-Flop Input Equations**

# Derivation of Flip-Flop Input Equations

□ Determine the flip flop input equations from the next-state equations using K-maps

- Always copy X's from next state maps onto input maps first
- Fill in the remaining squares with 0's

Type of FF	Input	Q = 0		Q = 1		Rules for forming input map from next state map	
		Q <sup>+</sup> = 0	Q <sup>+</sup> = 1	Q <sup>+</sup> = 0	Q <sup>+</sup> = 1	Q = 0 Half of Map	Q = 1 Half of Map
D	D	0	1	0	1	No change	No change
T	T	0	1	1	0	No change	Complement
S-R	S	0	1	0	X	No change	Replace 1's with X's
	R	X	0	1	0	Replace 0's with X's Replace 1's with 0's	Complement
J-K	J	0	1	X	X	No change	Fill in with X's
	K	X	X	1	0	Fill in with X's	Complement

# Important Tables

Q	Q <sup>+</sup>	D
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-Flop

Q	Q <sup>+</sup>	T
0	0	0
0	1	1
1	0	1
1	1	0

T Flip-Flop

Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

S-R Flip-Flop

Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

J-K Flip-Flop

# 3-Variable Example (1/3)

AB \ Q	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$Q^+$



AB \ Q	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$$D = Q'A'B + QB' + AB'$$

AB \ Q	0	1
00	0	0
01	1	1
11	0	1
10	1	X

$$T = A'B + AB' + QB$$

# 3-Variable Example (2/3)

AB \ Q		0	1
00	0	1	
01	1	0	
11	0	0	
10	1	X	

$Q^+$



AB \ Q		0	1
00	0	X	
01	1	0	
11	0	0	
10	1	X	

$S = AB' + Q'A'B$

AB \ Q		0	1
00	X	0	
01	0	1	
11	X	1	
10	0	X	

$R = QB$

# 3-Variable Example (3/3)

AB \ Q		0	1
00		0	1
01		1	0
11		0	0
10		1	X

$Q^+$



AB \ Q		0	1
00		0	X
01		1	X
11		0	X
10		1	X

$J = A'B + AB'$

AB \ Q		0	1
00		X	0
01		X	1
11		X	1
10		X	X

$K = B$



# 4-Variable Example (1/3)

BC \ Q <sub>1</sub> A		00	01	11	10
BC	00	0	1	0	1
	01	X	1	1	0
	11	1	X	X	1
	10	0	0	0	X

$Q_1^+$



BC \ Q <sub>1</sub> A		00	01	11	10
BC	00	0	1	1	0
	01	X	1	0	1
	11	1	X	X	0
	10	0	0	1	X

$T_1$

# 4-Variable Ex. (2/3)

CQ <sub>2</sub> \ AB				
	00	01	11	10
00	1	X	1	0
01	0	0	X	1
11	1	0	X	1
10	X	0	0	1

$Q_2^+$



CQ <sub>2</sub> \ AB				
	00	01	11	10
00	1	X	1	0
01	0	0	X	X
11	X	0	X	X
10	X	0	0	1

$S_2$

CQ <sub>2</sub> \ AB				
	00	01	11	10
00	0	X	0	X
01	1	1	X	0
11	0	1	X	0
10	X	X	X	0

$R_2$

# 4-Variable Ex. (3/3)

$Q_3C \backslash AB$	00	01	11	10
00	0	0	1	X
01	0	1	X	1
11	X	X	0	0
10	1	1	1	0

$Q_3^+$



$Q_3C \backslash AB$	00	01	11	10
00	0	0	1	X
01	0	1	X	1
11	X	X	X	X
10	X	X	X	X

$J_3$

$Q_3C \backslash AB$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	X	X	1	1
10	0	0	0	1

$K_3$

# Q&A

# Announcement (0513)

## ❑ Homework 3: grades will be announced soon

- We are holding 24 points before demo

## ❑ Homework 4: due at noon on Jun 3

- Lab 2 part will be announced next week

## ❑ Lab 2: May 20 (next week)

- Please bring your laptop
  - Our plan is that you can complete most of Lab 2 in the lecture time

## ❑ Plan from now

- May 20: Lab 2 + Short Talk by Prof. Jie-Hone Jiang
- May 27: Lecture (+ Short Talk by Prof. Chien-Mo Li)
- Jun 3: Lab 1 and Lab 2 Demo
- Jun 10: Lecture
- Jun 17: Final Exam